



CARIBBEAN EXAMINATIONS COUNCIL

CARIBBEAN ADVANCED PROFICIENCY EXAMINATION®

PHYSICS

UNIT 2 – Paper 02

2 hours 30 minutes

READ THE FOLLOWING INSTRUCTIONS CAREFULLY.

1. This paper consists of SIX questions in TWO sections. Answer ALL questions.
2. For Section A, write your answers in the spaces provided in this booklet.
3. For Section B, write your answers in the spaces provided at the end of each question in this booklet.
4. All working **MUST** be shown.
5. You may use a silent, non-programmable calculator to answer questions, but you should note that the use of an inappropriate number of figures in answers will be penalized.

COUVA EAST S. V. YEAR 1
LIBRARY
636-2585

C.E.S.E.C.

DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD TO DO SO.

NOTHING HAS BEEN OMITTED.

LIST OF PHYSICAL CONSTANTS

Speed of light in free space	c	=	$3.00 \times 10^8 \text{ m s}^{-1}$
Permeability of free space	μ_0	=	$4\pi \times 10^{-7} \text{ H m}^{-1}$
Permittivity of free space	ϵ_0	=	$8.85 \times 10^{-12} \text{ F m}^{-1}$
			$\frac{1}{4\pi \epsilon_0} = 9.0 \times 10^9 \text{ m F}^{-1}$
Elementary charge	e	=	$1.60 \times 10^{-19} \text{ C}$
Planck's constant	h	=	$6.63 \times 10^{-34} \text{ J s}$
Unified atomic mass constant (Energy equivalence:	u $1u$	= =	$1.66 \times 10^{-27} \text{ kg}$ 931 MeV/c^2)
Rest mass of electron	m_e	=	$9.11 \times 10^{-31} \text{ kg}$
Rest mass of proton	m_p	=	$1.67 \times 10^{-27} \text{ kg}$
Acceleration due to gravity	g	=	9.81 m s^{-2}
1 Atmosphere	Atm	=	$1.00 \times 10^5 \text{ N m}^{-2}$
Avogadro's constant	N_A	=	$6.02 \times 10^{23} \text{ per mole}$

GO ON TO THE NEXT PAGE

SECTION A

Answer ALL questions.

Write your answers in the spaces provided in this booklet.

1. (a) With the aid of a diagram, derive the formula for the equivalent resistance of two resistors in parallel.

[6 marks]

- (b) Figure 1A is a potential divider circuit which splits up the 32 V from the battery into voltages, V_1 and V_2 . Figure 1B is the equivalent circuit to Figure 1A.

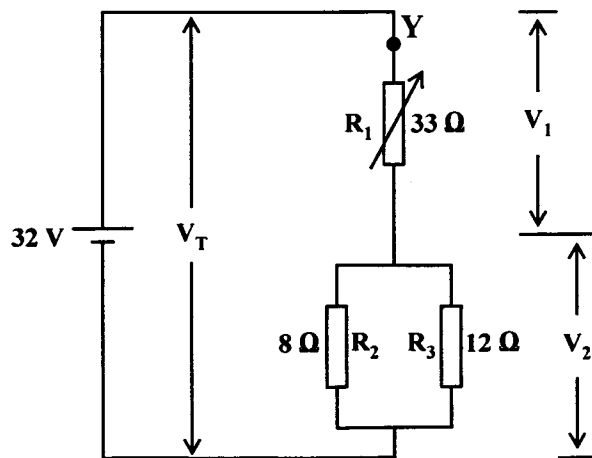


Figure 1A

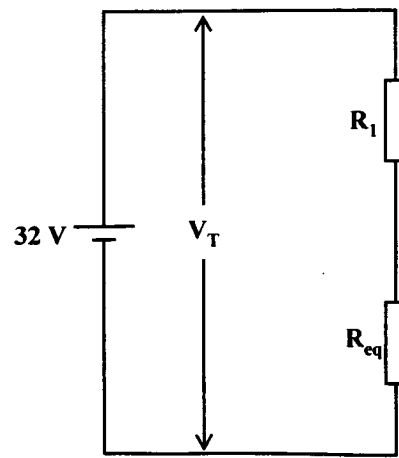


Figure 1B

GO ON TO THE NEXT PAGE

- (i) Calculate the equivalent resistance, R_{eq} in Figure 1B.

[2 marks]

- (ii) Determine the voltage, V_2 .

[1 mark]

- (c) The calculations above assume that the output resistance of the 32 V battery is zero. In practice this may not be so. In order to determine the internal resistance of the battery, an ammeter is inserted in the circuit at Y and the resistance of R_1 is reduced.

The terminal voltage, V_T , of the battery is monitored using a high resistance digital voltmeter. The readings of the ammeter (I) and the voltmeter (V_T) are recorded and tabulated. These are shown in Table 1 below.

TABLE 1

V_T/V	I/A
30	0.8
28	1.6
26	2.5
24	3.3
22	4.1

- (i) Use the results above to plot a graph of I against V_T on the grid provided on page 7. **[3 marks]**
- (ii) The slope, S , of the graph is related to the internal resistance, r , by $S = -\frac{1}{r} \Omega^{-1}$. Find S and hence determine the internal resistance, r , of the battery.

[3 marks]

Total 15 marks

GO ON TO THE NEXT PAGE

2. Figure 2 shows the gain-frequency curve (the gain-frequency response) of a general purpose operational amplifier (op-amp).

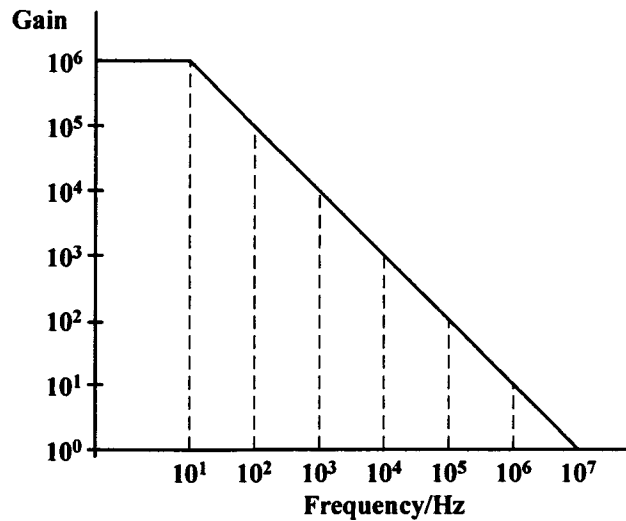


Figure 2

- (a) Use the graph to determine the
- (i) open loop d.c. gain of the amplifier
 - (ii) unity gain bandwidth of the amplifier
 - (iii) open loop bandwidth of the amplifier.

[1 mark]

[1 mark]

[1 mark]

GO ON TO THE NEXT PAGE

- (b) The op-amp with frequency response shown in Figure 2 is to be used as a non-inverting amplifier with the feedback resistance $R_f = 330 \text{ k}\Omega$ and input resistance $R_i = 3.3 \text{ k}\Omega$.

- (i) Draw the circuit diagram for this amplifier and label the resistors with their values.

[3 marks]

- (ii) Calculate the gain of the amplifier.

[2 marks]

- (iii) Use the open loop gain-frequency curve in Figure 2 to determine the closed loop bandwidth of this amplifier.

[2 marks]

- (iv) Deduce the gain of the amplifier when the input resistance is made infinitely large (so that it can be effectively removed from the circuit).

[2 marks]

- (v) What would be the input impedance of the resulting circuit?

[1 mark]

- (vi) Identify the practical application for the circuit and state why it is suited for this application.

[2 marks]

Total 15 marks

GO ON TO THE NEXT PAGE

3. (a) Describe the phenomenon of 'photoelectric emission'.

[3 marks]

- (b) Identify the property of a light source that would make it suitable for a demonstration of this phenomenon and give a reason why this property makes it suitable.

[2 marks]

- (c) Calculate the energy (in eV) of a light photon of wavelength 200 nm.

[3 marks]

- (d) The light source in Part (c) is used in a photoemission experiment with a metal whose work function is, $\Phi = 4.6 \text{ eV}$. Calculate the maximum velocity of the electrons ejected from the surface.

[3 marks]

- (e) The data in Table 2 were obtained for a photoemission experiment using Caesium.

TABLE 2

Stopping Potential V_s/V	Wavelength λ/nm
2.8	253
2.3	280
1.9	313
1.3	365
1.0	405

- (i) On the grid provided on page 13, plot a graph of V_s against λ . **Ensure that the λ scale extends to 550 nm.** [3 marks]
- (ii) From the graph determine the cut-off wavelength for Caesium.

[1 mark]

Total 15 marks

GO ON TO THE NEXT PAGE

1	2	3	999	1000
---	---	---	---	---	---	---	---	---	----	----	----	----	-----	-----	-----	-----	------

GO ON TO THE NEXT PAGE

SECTION B

Answer ALL questions.

Write your answers in the spaces provided at the end of each question.

4. (a) Figure 3 shows a model of an electron gun similar to that found in older television sets and oscilloscopes. Electrons from a thermionic emitter are accelerated to high velocities by the potential difference between the plates and pass through a small hole in the negative plate.

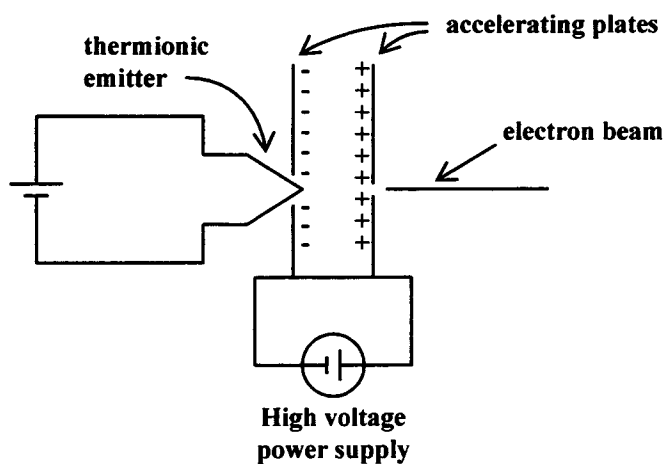


Figure 3

- (i) By equating the gain in kinetic energy of the electrons to the work done in accelerating them, show that the velocity, v_e , of the emerging beam electrons is given by:

$$v_e = \sqrt{\frac{2e V_p}{m_e}}$$

where V_p is the potential difference between the plates.

- (ii) Calculate the velocity of the electrons in the emerging electron beam when $V_p = 25 \text{ kV}$. [4 marks]

GO ON TO THE NEXT PAGE

- (b) Figure 4 shows a long solenoid which has 1000 turns per metre and carries a current of 10 A.

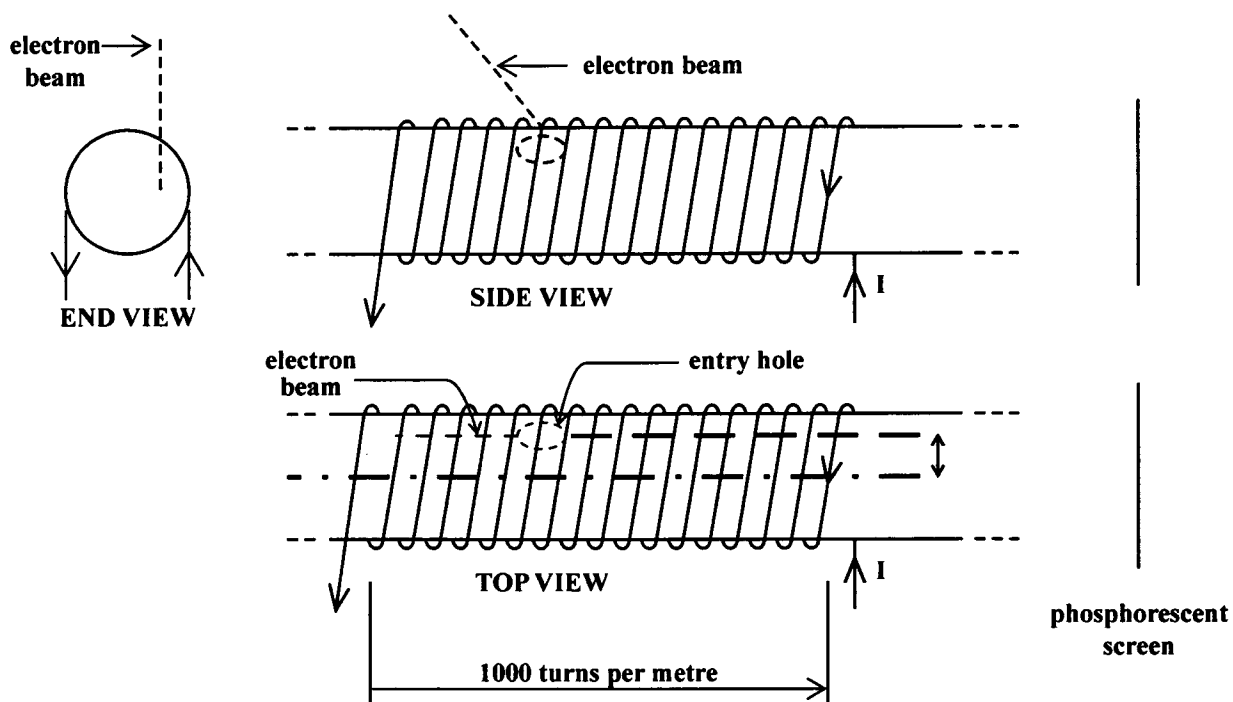


Figure 4

- (i) Calculate the magnitude and direction of the magnetic field inside the solenoid.
[3 marks]
- (ii) The solenoid is placed with its long axis horizontal so that a tiny hole (shown exaggerated in the diagram) faces upward and is displaced from the axis by a radial distance X . An electron beam is directed through the hole as shown in Figure 4.
 - a) Explain the effect on the electron's **horizontal** velocity component, resulting from its interaction with the B-field.
 - b) Describe the effect on the electron's **vertical** velocity component.
 - c) Describe the resultant motion of the electrons and the nature of the image produced on the phosphorescent screen when the B-field is large enough to prevent the electrons from touching the interior of the solenoid.

[8 marks]

Total 15 marks

GO ON TO THE NEXT PAGE

[illegible]

Write the answer to Question 4 here.

This image shows a single sheet of white paper with horizontal ruling lines. The lines are evenly spaced and run across the width of the page. There are no margins, text, or other markings on the paper.

This image shows a single sheet of white paper with horizontal ruling lines. The lines are evenly spaced and run across the width of the page. There are no margins, text, or other markings on the paper.

5. Some modern cars incorporate an electronic system for turning on the headlights automatically whenever the light levels of the surroundings fall below a certain threshold. Other specifications of this type of system are:

- the lights can only come ON if the ignition switch S1 (logic A) is ON
- the headlights AUTO switch S2 (logic B) must be ON for the lights to come ON
- lighting level (logic C) below threshold is to be taken as logic 0

- (a) Use logic Y to represent the output of this system and draw up the truth table for the operation of the headlight automatic switching circuit. Write the logic equation represented by this truth table. **[3 marks]**

- (b) The circuit shown in Figure 5 is proposed for implementing the headlight auto switching system.

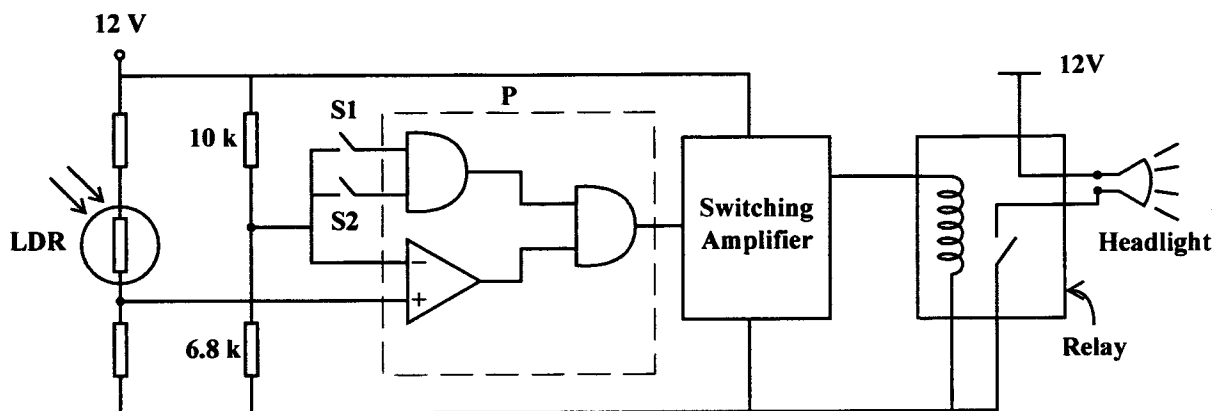


Figure 5

- (i) In this circuit, the open loop operational amplifier is used to compare the surrounding lighting level with a preset value. Explain how this is done.
- (ii) Justify the need for the light dependent resistor (LDR) in the circuit.
- (iii) Describe how a relay functions, stating why this device is necessary in the circuit. **[7 marks]**
- (c) (i) Replace the circuit in the dashed box, P, with one consisting of NAND gates only.
- (ii) The 7400 chip has 4 NAND gates. How many 7400 chips are required for the NAND-equivalent circuit drawn in Part c (i) ? **[5 marks]**

Total 15 marks

GO ON TO THE NEXT PAGE

This image shows a single sheet of white paper with horizontal ruling lines. The lines are evenly spaced and run across the width of the page. There are no margins, text, or other markings on the paper.

This image shows a single sheet of white paper with horizontal ruling lines. The lines are evenly spaced and run across the width of the page. There are no margins, text, or other markings on the paper.

02238020/CAPE 2013

[illegible][illegible]

6. (a) A radioactive sample initially contains N_0 radioactive particles. Its decay constant is λ and it decays to N particles in time, t . Write the equation describing this decay. [1 mark]

- (b) A capacitor, C , initially charged to voltage, V_0 , will discharge through a resistance, R , according to the equation $V = V_0 \exp(-t/\tau)$, where τ is called the time constant.

- (i) Write the equation expressing τ , in terms of R and C .
- (ii) If the capacitive discharge is used to model radioactive decay, where voltage is the analogue of number of particles, what would be the relationship between time constant, τ and decay constant, λ ?
- (iii) Given that $t_{1/2}$ is the half-life of a radioactive sample, use the decay equation from

Part (a) to show that $t_{1/2} = \frac{0.69}{\lambda}$. [5 marks]

- (c) The circuit shown below is used to model the decay of the radioactive isotope Francium-221, which has a half-life of 288 s. S_1 is initially switched to terminal a .

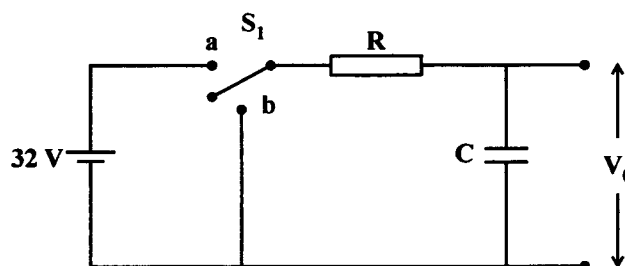


Figure 6

- (i) Describe the change in the voltages across R and C , both of which initially had no voltage across them.
- (ii) After a sufficiently long time, the voltages across R and C become fairly stable and S_1 is then switched to terminal b , so that the voltage across C models the decay of the Francium-221 isotope. Using a value of $R = 1 \text{ M}\Omega$, calculate the value of C needed to model the radioactive decay of Francium-221. [6 marks]

- (d) (i) State what is meant by the term 'activity' of a radioactive nucleus and write its expression in mathematical form.

- (ii) A sample of Francium-221 contains 10^{12} atoms. Calculate its activity. [3 marks]

Total 15 marks

GO ON TO THE NEXT PAGE

Write the answer to Question 6 here.

This image shows a single sheet of white paper with horizontal ruling lines. The lines are evenly spaced and run across the width of the page. There are no margins, text, or other markings on the paper.

This image shows a single sheet of white paper with horizontal ruling lines. The lines are evenly spaced and run across the width of the page. There is no handwriting or other markings on the paper.

IF YOU FINISH BEFORE TIME IS CALLED, CHECK YOUR WORK ON THIS TEST.